



CPE241 Digital Logic Design  
 Final Exam Fall 2024

Instructor: Dr. Babar Mansoor  
 Max Marks: 50  
 Time Allowed: 03 Hours

Class: BCE 3B  
 Date: 18-01-2025

Q(1)[CLO3](5 Marks)

Analyze the following circuit shown in Figure 1 to express the functions  $F_1$  and  $F_2$  in terms of the inputs  $A, B$  and  $C$ . What is the relationship between  $F_1$  and  $F_2$ ?

 


Figure 1. Circuit for Question 1

Q(2)[CLO4](10 Marks)

- (5 Marks) Design a combinational circuit with minimum number of gates to convert a 3-bit input binary number into its equivalent Gray code.
- (5 Marks) Design a 3-bit magnitude comparator circuit for two binary numbers  $A = a_2a_1a_0$  and  $B = b_2b_1b_0$  as inputs. The required circuit has three outputs namely **EQ** (if  $A=B$ ), **GT** (if  $A>B$ ) and **LT** (if  $A<B$ ).

Q(3) [CLO3](5 Marks)

Analyze the behavior of a positive edge triggered JK flip flop by deriving its state transition table, next state equations and state diagram. Also write down the excitation table of a JK flip flop.

Q(4)[CLO3] (10 Marks)

Consider the sequential circuit shown in Figure 2. Analyze this circuit by deriving:

- State transition and output equations,
- State transition table,
- State diagram.
- Draw a timing diagram for the input sequence  $X=0110010$

0	0
0	1
1	0
1	1

 


Figure 2. Circuit for Question 4

Q(5) [CLO4](10 Marks)

Design a Mealy system whose output is 1 for every third 1 input (**not necessarily consecutive**). For example, if  $X$  is the input and  $Z$  is the output of the detector, then a sample pattern of  $X$  and  $Z$  is shown below:

$X$	0	1	1	1	1	1	1	0	1	1	0	1	0	0	0	1	0	1
$Z$	0	0	0	1	0	0	1	0	0	0	1	0	0	0	0	0	0	0

Design the circuit using D type flip flops.

Q(6) [CLO4](10 Marks)

- (7 Marks) Design a 2-bit Up/Down counter with two inputs:  $E$  (Enable) and  $U$  (Up). If  $E = 0$  then counter remains in the same state (regardless of  $U$ ). If  $EU = 11$  then count up from 0 to 3, then back to 0. If  $EU = 10$  then count down from 3 down to 0, then back to 3. The circuit should be designed using T flip flops.
- (3 Marks) Design a bit-serial adder to add two 4-bit binary numbers  $A$  and  $B$  and store the sum in a register. Use D flip flops.